

<b>Course Name:</b>	<b>Elements of Electrical and Electronics Engineering Laboratory</b>	<b>Semester:</b>	<b>I/II</b>
<b>Date of Performance:</b>	7 / 10 / 2024	<b>Batch No:</b>	C4 (01)
<b>Student Name:</b>	RAMESH S. PATEL	<b>Roll No:</b>	16010124224
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	/ 20

### Experiment No: 3

#### Title: Thevenin's Theorem & Norton's Theorem


##### Aim and Objective of the Experiment:

- To Verify for Thevenin's Theorem for the circuit
- To Verify Norton Theorem for the Circuit.

##### COs to be achieved:


CO1: Analyze resistive networks excited by DC sources using various network theorems.

##### Circuit Diagram:

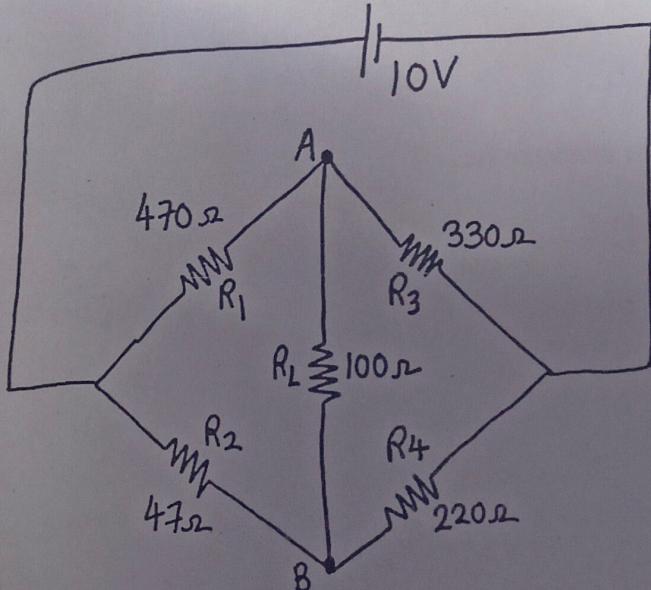





**Task 1: Circuit Diagram to measure  $R_{TH}/R_N$ :**

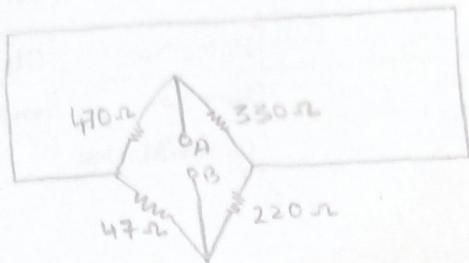

**Task 2: Circuit Diagram to measure  $V_{TH}$ :**

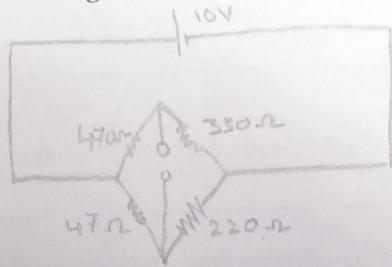

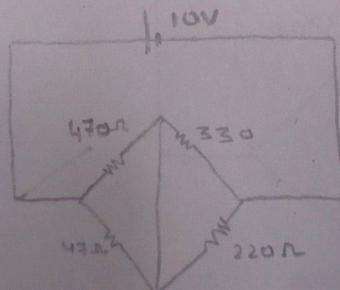**Task 3: Circuit Diagram to measure  $I_{SC}$ :**



### Stepwise-Procedure:

#### Thevenin's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set 10V and measure open circuit voltage  $V_{Th}$  across load terminals A and B.
3. Replace all voltage sources by Short circuit and measure  $R_{Th}$  across terminals A and B as per the circuit diagram shown in the figure.
4. Draw Thevenin's equivalent circuit and determine the value of load current from it.
5. Verify the results theoretically.

#### Norton's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set the voltages 10V
3. Remove the load resistance and measure the short circuit current  $I_{SC}$  through A and B terminals.
4. Replace all the voltage sources by Short circuit and measure  $R_{Th}$  across terminals A and B as per the circuit diagram shown in the figure.
5. Draw Norton's equivalent circuit and determine the value of load current.
6. Verify the results theoretically

#### Calculations:

Applying KVL or mesh ①

$$-10 - 330I_1 - 470I_2 = 0$$

$$-10 - 800I_2 = 0$$

$$-80I_2 = 1$$

$$I_2 = -1/80 = 0.0125 \text{ A}$$

Applying KVL or mesh ②

$$-470(I_2 - I_1) - 330(I_2 - I_1) - (220 + 47)I_2 = 0$$

$$800I_1 - 800I_2 - 267I_2 = 0$$

$$-10 - 1067I_2 = 0$$

$$I_2 = -10/1067 = 9.372 \times 10^{-3}$$

$$= 0.009372 \text{ A}$$

Using Norton's theorem

Applying KVL on loop ①

$$-47I_1 - 470(I_1 - I_3) = 0 \quad (i)$$

Applying KVL on loop (2)

$$-330(I_2 - I_3) - 220I_2 = 0 \quad (ii)$$

Applying KVL on loop (3)

$$-10 - 470(I_3 - I_1) - 330(I_3 - I_2) = 0 \quad (iii)$$

From (i), (ii) & (iii)


$$I_1 = 0.0520A, I_2 = 0.0343A, I_3 = 0.0572A$$

$$I_{sc} = I_1 - I_2 = -0.0149A = -17.7mA$$


Observation Table:

	$V_{TH}$ (V)	$R_{TH} / R_N$ ( $\Omega$ )	$I_N$ (mA)	$I_L$ (mA)
Theoretical value	- 4.1 V	232.60 $\Omega$	-17.68 mA	-12.3 mA
Practical value	- 4.05 V	228 $\Omega$	-17.5 mA	-13.5 mA

Draw Thevenin's Equivalent circuit

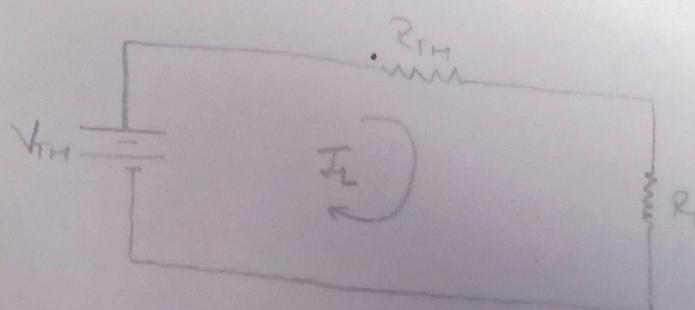

Draw Norton's Equivalent circuit

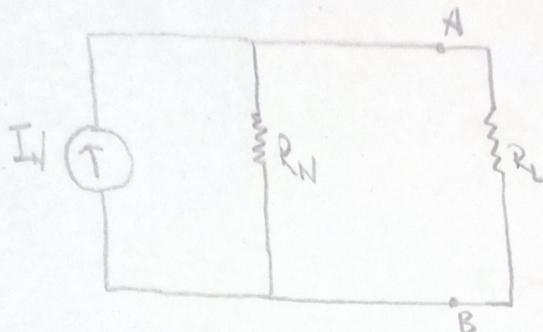

**Conclusion:**

The following experiment helps us in understanding the steps to verify Thevenin's & Norton's theorem for the circuit. Thevenin resistance & Norton resistance are eq. Any linear circuit can be simplified to an equivalent circuit consisting of a single voltage source with a series resistance connected to the load. The exp also helped us to examine resistive networks excited by DC sources using various network theorems.

Signature of faculty in-charge with Date: