

Course Name:	EEEEEL	Semester:	I/II
Date of Performance:	22 / 11 /2024	Batch No:	C4-1
Student Name:	Ramesh Patel	Roll No:	16010124224
Faculty Sign & Date:		Grade/Marks:	/20

**Experiment No: 8 Title: BJT Common
Emitter Characteristics**

Aim and Objective of the Experiment:
<ul style="list-style-type: none"> To understand the structure and working of Bipolar Junction Transistor To plot the Common Emitter characteristics of a BJT
COs to be achieved:
CO5: Understand Bipolar Junction transistor and its applications.
Requirements:
PC with internet facility
Link for virtual lab: https://be-iitkgp.vlabs.ac.in/exp/common-emitter-characteristics/
Theory:
<p>Structure of Bipolar Junction Transistor</p> <p>A bipolar junction transistor, BJT, is a single piece of silicon with two back-to-back P-N junctions. BJTs can be made either as PNP or as NPN. They have three regions and three terminals, emitter, base, and collector represented by E, B, and C respectively.</p> <p>Emitter (E): It is the region to the left end which supply free charge carriers i.e., electrons in n-p-n or holes in p-n-p transistors. These majority carriers are injected to the middle region i.e. electrons in the p region of n-p-n or holes in the n region of p-n-p transistor. Emitter is a heavily doped region to supply a large number of majority carriers into the base.</p> <p>Base (B): It is the middle region where either two p-type layers or two n-type layers are sandwiched. The majority carriers from the emitter region are injected into this region. This region is thin and very lightly doped.</p>

Collector (C): It is the region to right end where charge carriers are collected. The area of this region is largest compared to emitter and base region. The doping level of this region is intermediate between heavily doped emitter region and lightly doped base region.

Input Characteristics

It is the plot of the base current, I_B , versus the base-emitter voltage, V_{BE} , for various values of the collector-emitter voltage, V_{CE} for constant V_{CE}

Output Characteristics

It is the plot of the collector current, I_C , versus the collector-emitter voltage, V_{CE} , for various values of the base current, I_B

Circuit Diagram/ Block Diagram:

BJT Common Emitter - Input Characteristics

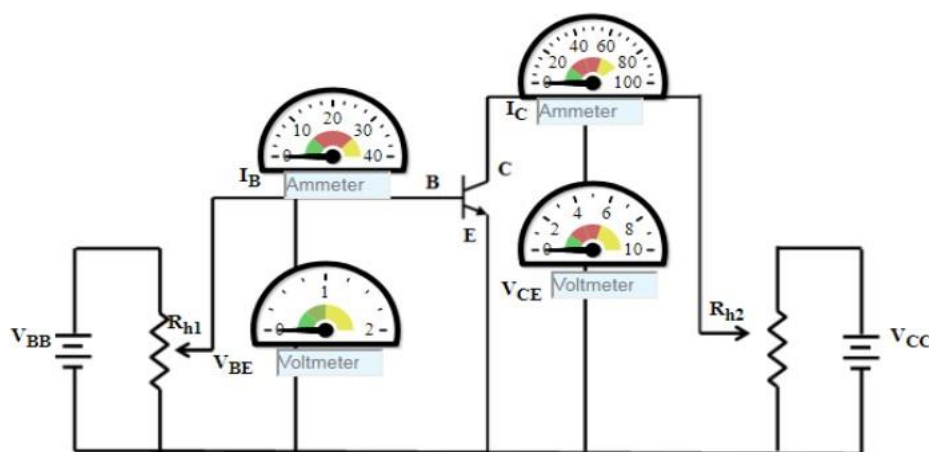


Figure:1

BJT Common Emitter - Output Characteristics

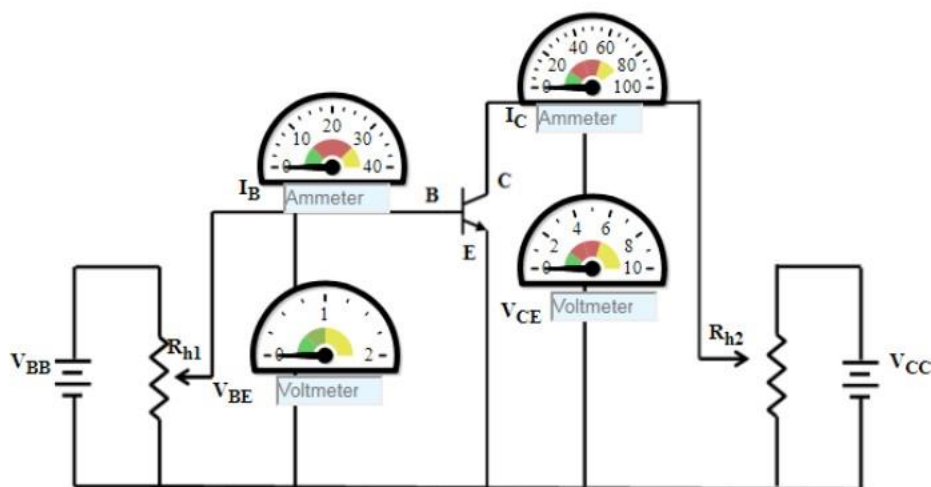


Figure: 2

Stepwise-Procedure:

BJT Common Emitter - Input Characteristics

1. Initially set rheostat $R_{h1} = 1 \Omega$ and rheostat $R_{h2} = 1 \Omega$
2. Set the Collector-Emitter Voltage(V_{CE}) to 1 V by adjusting the rheostat R_{h2}
3. Base Emitter Voltage(V_{BE}) is varied by adjusting the rheostat R_{h1} .
4. Note the reading of Base current(I_B) in micro Ampere.
5. Click on 'Plot' to plot the I-V characteristics of Common-Emitter configuration. A graph is drawn with V_{BE} along X-axis and I_B along Y-axis.
6. Click on 'Clear' button to take another sets of readings
7. Now set the Collector-Emitter Voltage(V_{CE}) to 2 V, 3 V, 4 V

BJT Common Emitter - Output Characteristics

1. Initially set rheostat $R_{h1} = 1 \Omega$ and rheostat $R_{h2} = 1 \Omega$
2. Set the Base current(I_B) 15 μA by adjusting the rheostat R_{h1}
3. Vary the Collector-Emitter Voltage(V_{CE}) is varied by adjusting the rheostat R_{h2} .
4. Note the reading of Collector current(I_C).
5. Click on 'Plot' to plot the I-V characteristics of Common-Emitter configuration. A graph is drawn with V_{CE} along X-axis and I_C along Y-axis.
6. Click on 'Clear' button to take another sets of readings

7. Now set the Base Current(I_B) to 20 μ A

V-Lab Screen shots

BJT- CE INPUT CHARACTERISTICS

INSTRUCTION

EXPERIMENTAL TABLE

Serial No.	Collector-Emitter Voltage	
	Base-Emitter Voltage V	Base Current(μ A)
1	0.1000	2.326
2	0.2000	2.680
3	0.3000	3.089
4	0.4000	3.560
5	0.5000	4.104
6	0.6000	4.732
7	0.7000	5.455
8	0.8000	6.290
9	0.9000	7.253
10	1.0000	8.364
11	1.2000	11.12
12	1.4000	14.80
13	1.6000	19.68
14	1.8000	26.19


CONTROLS

R_{h1} Ohms
 R_{h2} Ohms

Add to Table Plot Clear


Print It

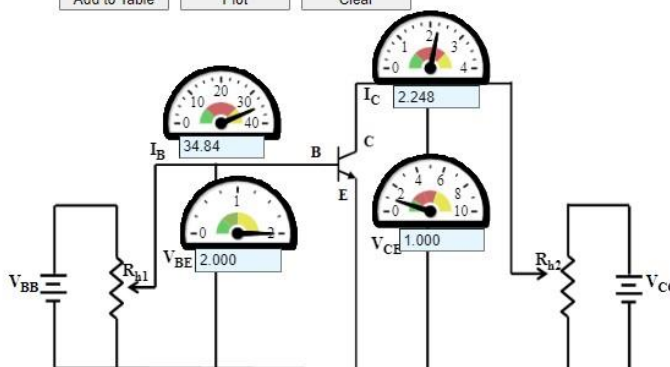Take another sets of Base-Emitter and Base Current readings for another Collector-Emitter value



GRAPH PLOT

V-I Plot

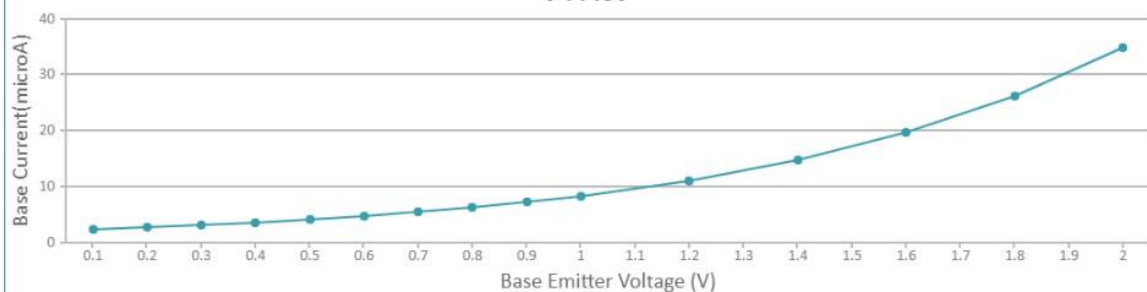

BJT- CE INPUT CHARACTERISTICS


INSTRUCTION		
EXPERIMENTAL TABLE		
Serial No.	Collector-Emitter Voltage 2.000 V	
	Base-Emitter Voltage V	Base Current(μ A)
1	0.1000	2.335
2	0.2000	2.690
3	0.3000	3.098
4	0.4000	3.570
5	0.5000	4.114
6	0.6000	4.741
7	0.7000	5.465
8	0.8000	6.300
9	0.9000	7.263
10	1.0000	8.374
11	1.2000	11.13
12	1.4000	14.81
13	1.6000	19.69
14	1.8000	26.20

CONTROLS


R_{b1} Ohms
 R_{b2} Ohms

Print It

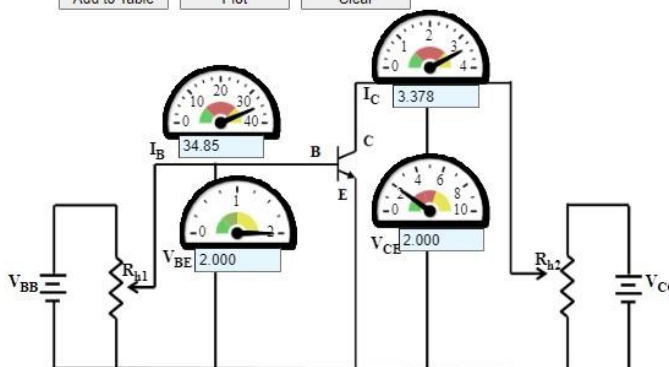Take another sets of Base-Emitter and Base Current readings for another Collector-Emitter value



GRAPH PLOT

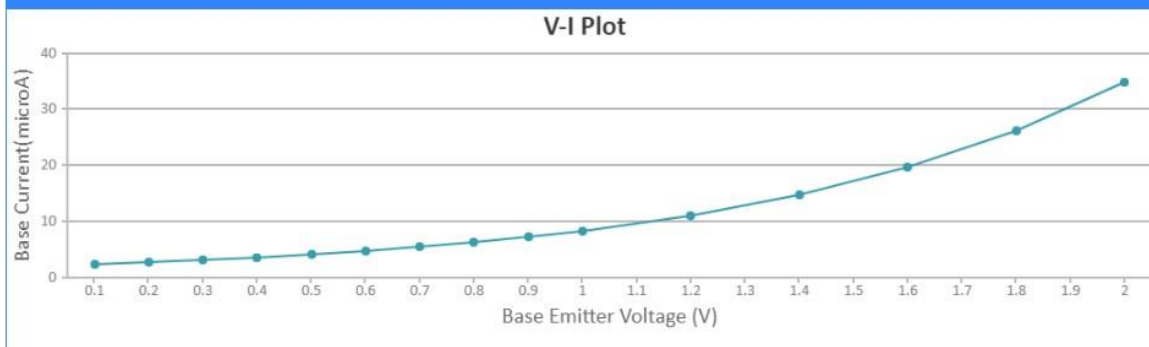

BJT- CE INPUT CHARACTERISTICS

INSTRUCTION

EXPERIMENTAL TABLE


Serial No.	Collector-Emitter Voltage	
	Base-Emitter Voltage V	Base Current(μ A)
1	0.1000	4.011
2	0.2000	4.365
3	0.3000	4.774
4	0.4000	5.246
5	0.5000	5.789
6	0.6000	6.417
7	0.7000	7.141
8	0.8000	7.975
9	0.9000	8.939
10	1.0000	10.05
11	1.200	12.81
12	1.400	16.48
13	1.600	21.37
14	1.800	27.87

CONTROLS

R_{h1} Ohms
 R_{h2} Ohms


Print It

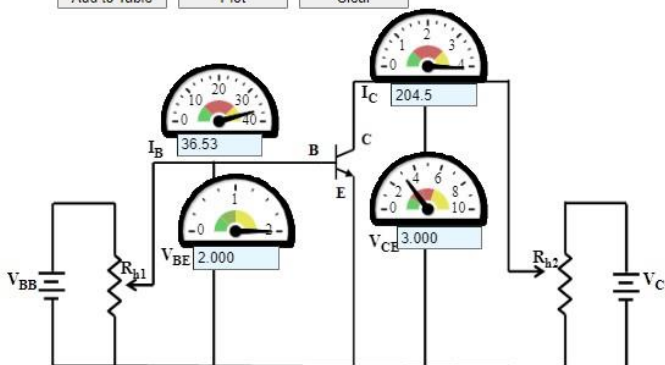Take another sets of Base-Emitter and Base Current readings for another Collector-Emitter value



GRAPH PLOT

V-I Plot

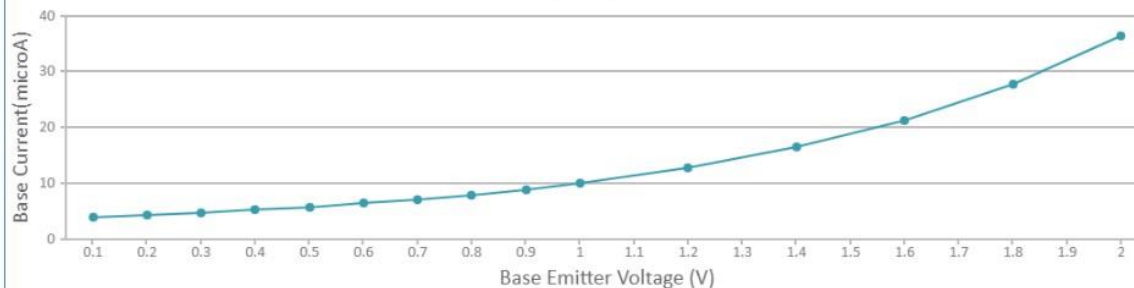

BJT- CE OUTPUT CHARACTERISTICS

INSTRUCTION

EXPERIMENTAL TABLE

Serial No.	Base-Current 15.35 μ A	
	Collector-Emitter Voltage V	Collector Current mA
1	0.1000	5.994
2	0.2000	11.87
3	0.3000	17.52
4	0.4000	22.85
5	0.5000	27.79
6	1.000	45.81
7	2.000	57.98
8	4.000	60.10
9	5.000	60.14
10	6.000	60.14
11	8.000	60.14
12	10.00	60.14

CONTROLS

R_{h1} Ohms
 R_{h2} Ohms


Add to Table

Plot

Clear


Print It

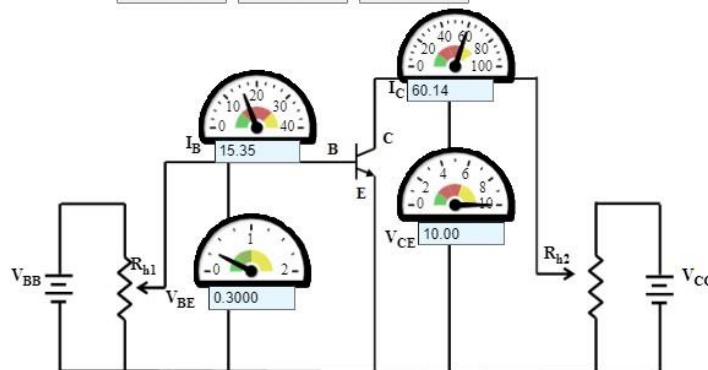Take another sets of Collector-Emitter and Collector Current readings for another Base Current



GRAPH PLOT

V-I Plot

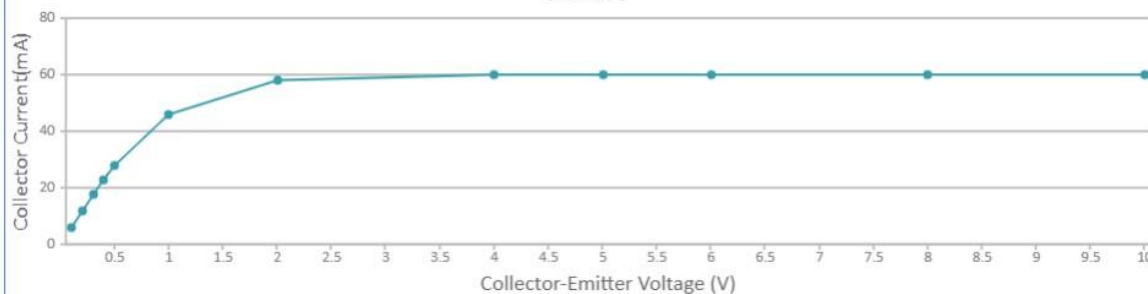

BJT- CE OUTPUT CHARACTERISTICS


INSTRUCTION		
EXPERIMENTAL TABLE		
Serial No.	Base-Current 20.43 μ A	
	Collector-Emitter Voltage V	Collector Current mA
1	0.1000	9.202
2	0.2000	18.22
3	0.3000	26.90
4	0.4000	35.08
5	0.5000	42.66
6	1.000	70.31
7	2.000	89.00
8	4.000	92.26
9	6.000	92.32
10	8.000	92.32
11	10.00	92.32

CONTROLS


R_{h1} Ohms
 R_{h2} Ohms

Print It

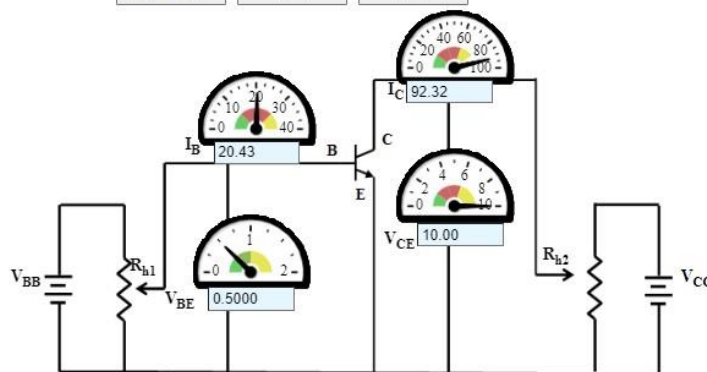Take another sets of Collector-Emitter and Collector Current readings for another Base Current



GRAPH PLOT

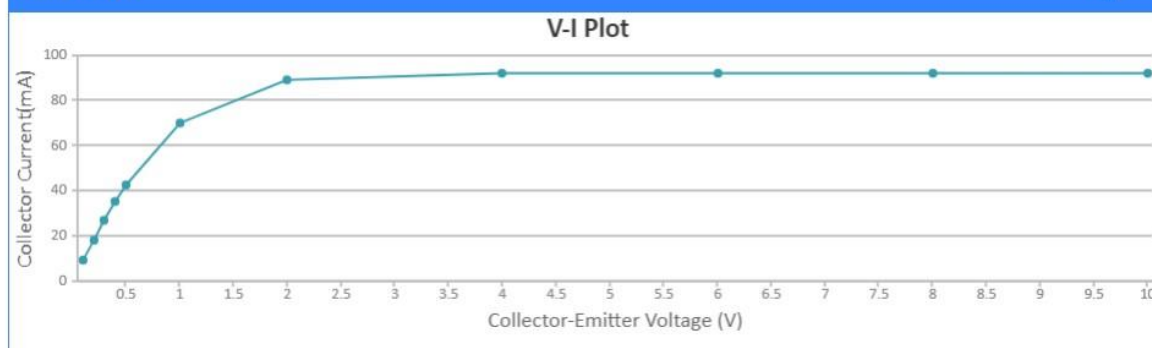

BJT- CE OUTPUT CHARACTERISTICS

INSTRUCTION

EXPERIMENTAL TABLE

Serial No.	Base-Current	
	Collector-Emitter Voltage V	Collector Current mA
1	0.1000	12.96
2	0.2000	25.67
3	0.3000	37.89
4	0.4000	49.42
5	0.5000	60.11
6	1.000	99.07
7	2.000	125.4
8	4.000	130.0
9	6.000	130.1
10	8.000	130.1
11	10.00	130.1

CONTROLS

R_{h1} Ohms
 R_{h2} Ohms


Add to Table

Plot

Clear


Print It

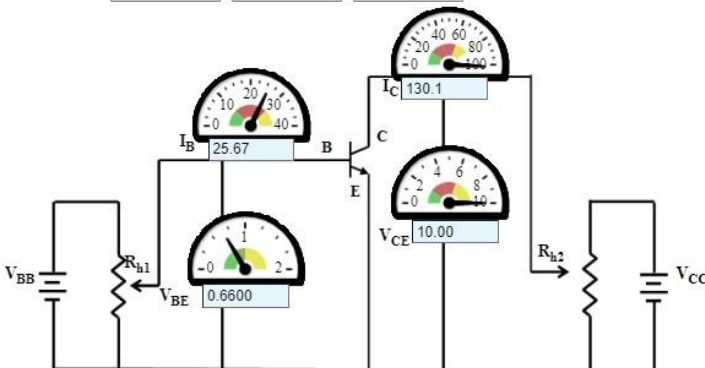Take another sets of Collector-Emitter and Collector Current readings for another Base Current



GRAPH PLOT

V-I Plot

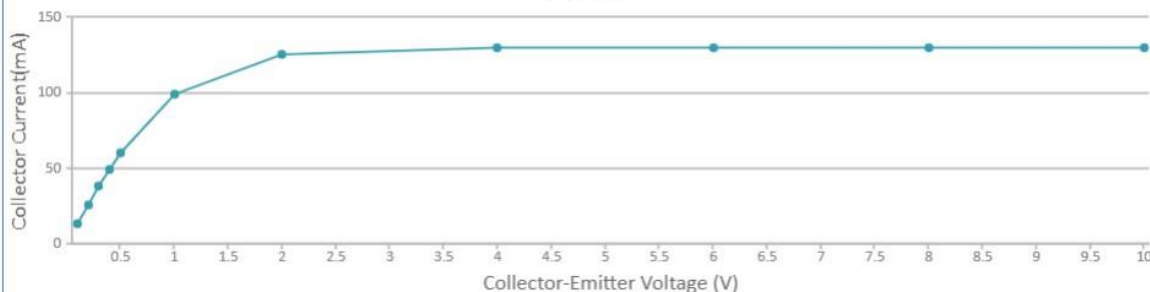

Post Lab Subjective/Objective type Questions:
<p>1. Explain the structure of a BJT and the current relationships of the BJT CE amplifier</p> <p>A bipolar junction transistor (BJT) is a semiconductor device that amplifies current and is made up of three doped regions and two P-N junctions:</p> <p style="margin-left: 40px;">Emitter: The left-most region that supplies majority carriers, such as electrons in an NPN transistor or holes in a PNP transistor</p> <p style="margin-left: 40px;">Base: The middle region that receives majority carriers from the emitter</p> <p style="margin-left: 40px;">Collector: The right-most region that collects charge carriers</p> <p>2. Draw and explain the various regions of operation of the BJT amplifier</p>
Conclusion:

Signature of faculty in-charge with Date: