



Course Name:	Elements of Electrical and Electronics Engineering Laboratory	Semester:	I/II
Date of Performance:	30/09/2024	Batch No:	C4(01)
Student Name:	RAMESH. S. PATIL	Roll No:	16010124224
Faculty Sign & Date:		Grade/Marks:	/ 20

Experiment No: 2

Title: Mobile Battery Charger

Aim and Objective of the Experiment:

- To understand the working of Mobile Battery Charging Circuit
- To implement the circuit of Mobile Battery charger on Breadboard and observe the waveforms at various points (Input and output Waveforms for Bridge Rectifier) and measure the output voltage


COs to be achieved:



- CO1:** Analyze resistive networks excited by DC sources using various network theorems.
CO2: Demonstrate and analyze steady state response of single phase and three phase circuits
CO3: Understand principles and working of AC and DC machines with their applications.
CO4: Explain rectifier-filter circuits using PN junction diode and voltage regulator circuits using Zener diode

Requirements:

Step-down Transformer (6V-0-6V), Diodes(1N4007), voltage regulator IC 7805, Resistor, Capacitors, CRO, Digital Multimeter (DMM), breadboard, connecting wires, Micro USB cable, etc.

Circuit Diagram:

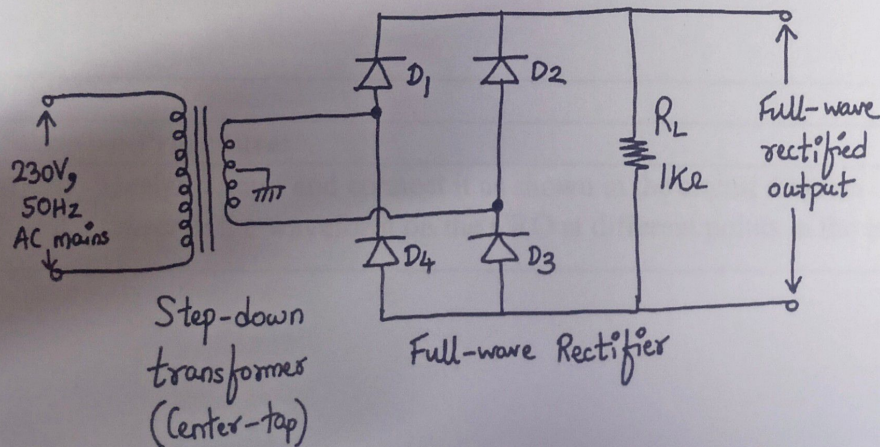

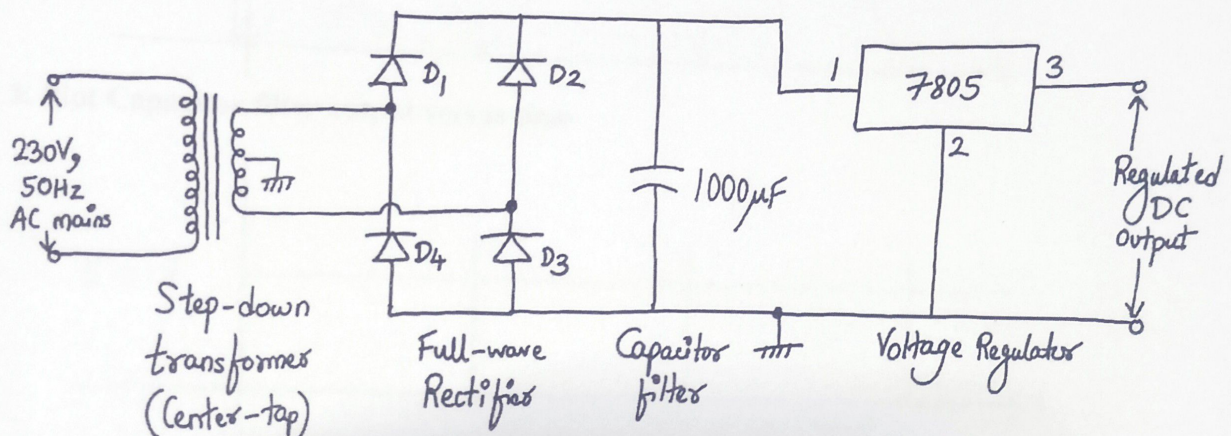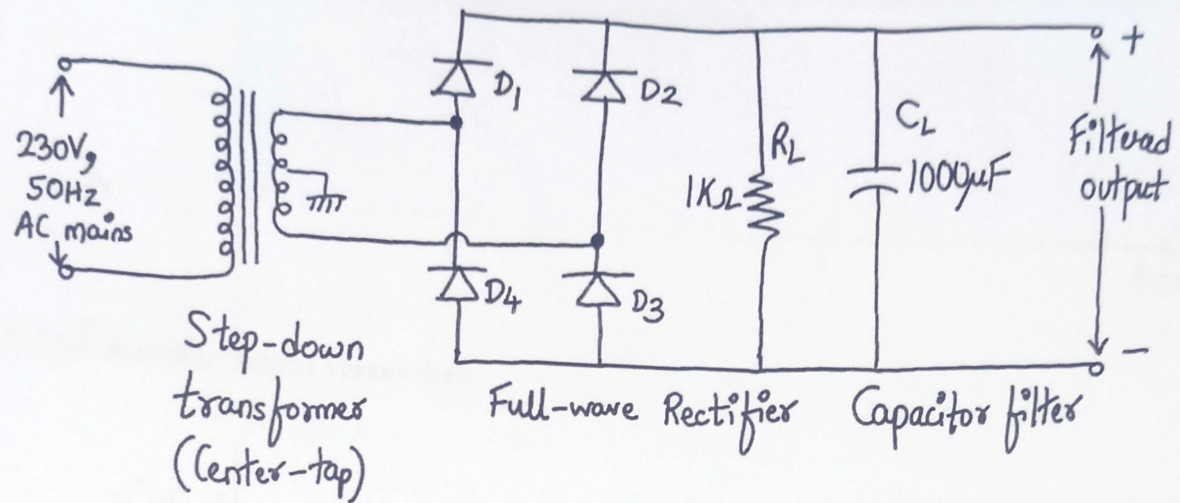

Mobile Battery Charger Circuit


Stepwise-Procedure:

1. Design circuit and connect it as shown in the circuit diagram
2. Observe the waveform on the CRO at different points in the circuits.




Output waveforms observed on CRO:

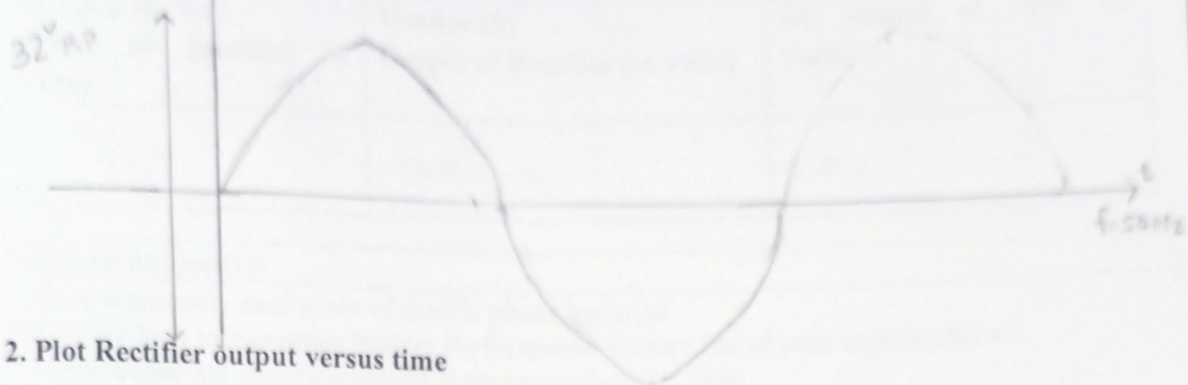
1. Plot secondary voltage across transformer versus time




2. Plot Rectifier output versus time

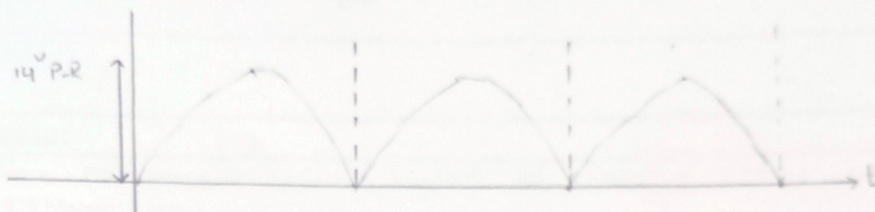

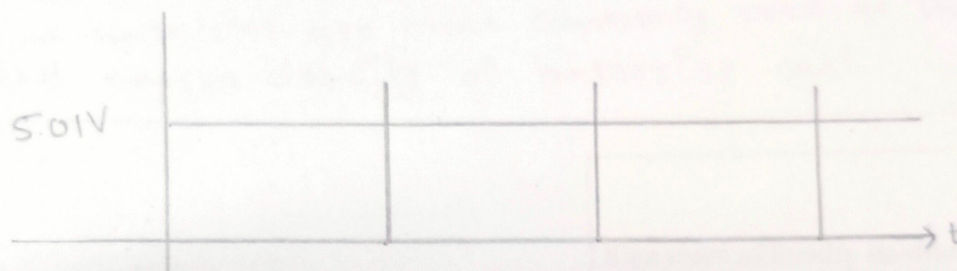3. Plot Capacitor filter output versus time



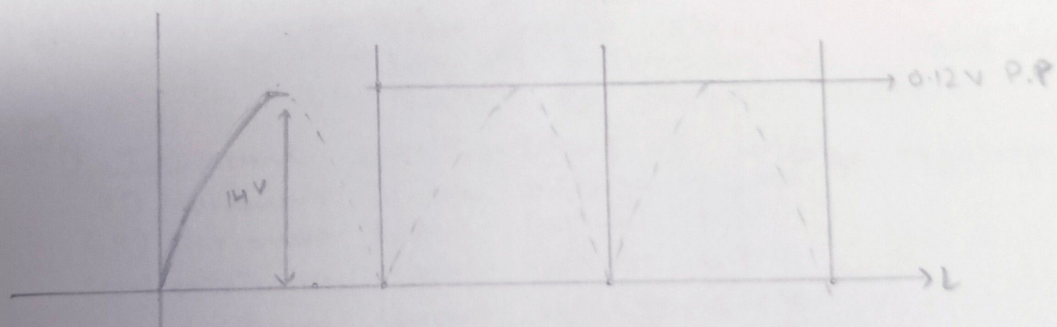4. Plot output of Voltage regulator versus time



Observation Table:

Vin (p-p & rms) (input of Rectifier in Volts)	Vout(peak) Output of Rectifier (in Volts)	DC output of 7805 (in Volts)
32V	14V	5.0V

Post Lab Subjective:

1. State commonly used types of mobile phone batteries
2. Explain how to maximize Battery Performance/ Battery life of your mobile phone?
3. Write important specifications of Voltage regulator IC 7805
(You can attach data sheet of IC 7805)

Conclusion:

Ans(i) The commonly used types of mobile phone batteries are:

- Lithium ion
- Lithium polymer
- Nickel Cadmium.

Lithium batteries are more commonly used as they allow highest energy density of batteries cell.

Signature of faculty in-charge with Date:

Ans(ii) You can maximize your battery performance by following these steps:-

- (i) Turn on Power Saving Mode
- (ii) Reduce Screen Brightness
- (iii) Turn off background app actions and updates.
- (iv) Switch to Airplane Mode.

Ans(iii) Important specifications of voltage Regulator IC 7805 are:-

- (i) Minimum Input Voltage: 7V
- (ii) Maximum Input Voltage: 35V
- (iii) Minimum Output Voltage: 4.8V
- (iv) Maximum Output Voltage: 5.2V
- (v) Current Rating: 1A
- (vi) Dimensions: 30x15x5mm