



SOMAIYA
VIDYAVIHAR UNIVERSITY

K J Somaiya College of Engineering

K. J. Somaiya College of Engineering, Mumbai-77
(A Constituent College of Somaiya Vidyavihar University)
Department of Sciences and Humanities



Course Name:	Elements of Electrical and Electronics Engineering Laboratory	Semester:	I/II
Date of Performance:	8/11/2024	Batch No:	C4-01
Student Name:	RAMESH. S. PATEL	Roll No:	16010124224
Faculty Sign & Date:		Grade/Marks:	/ 20

Experiment No: 7

Title: Measurement of Power using Two Wattmeter Method


Aim and Objective of the Experiment:

- To measure the power of three phase power using Two Wattmeter Method

COs to be achieved:

CO2: Demonstrate and analyze steady state response of single phase and three phase circuits

Circuit Diagram:

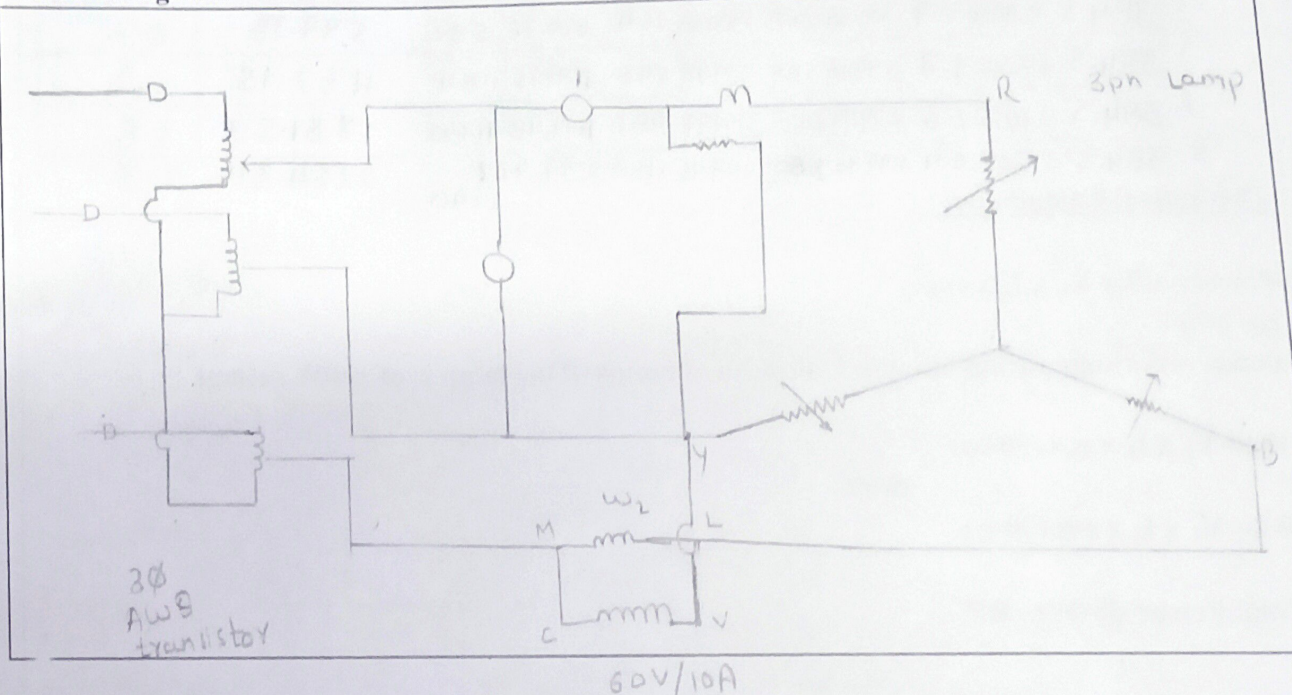



SOMAIYA
VIDYAVIHAR UNIVERSITY

K J Somaiya College of Engineering

K. J. Somaiya College of Engineering, Mumbai-77
(A Constituent College of Somaiya Vidyavihar University)
Department of Sciences and Humanities



Stepwise-Procedure:

1. Connect the circuit as shown in circuit diagram
2. Increase the load and note down the reading V_L, I_L, W_1 and W_2
3. Practically you will obtain total power $W = W_1 + W_2$
4. Theoretically power is measured by using formula $P = \sqrt{3} V_L I_L \cos \phi$,
using $\cos \phi = 1$ (unity) for resistive load.

Observation Table:

Sr.no	V_L (Volts)	I_L (Amp)		W_1 (KW)		W_2 (KW)		$W = (W_1 + W_2)$ (KW)		$P = \sqrt{3} V_L I_L \cos \phi$ (KW)	Lamp load given from lamp bank (KW)
		TH	PR	TH	PR	TH	PR	TH	PR		
1	384.5	0	0	0	0	0	0	0	0	0	0
2	384.5	0.9021	0.9	300.38	268	300.38	264	570.76	532	599.38	0.6
3	384.5	1.8018	1.7	599.98	588	599.98	596	1199.96	1184	1132.15	1.2
4	384.5	2.7028	2.6	899.99	860	899.99	880	1799.98	1740	1731.53	1.8
5	384.5	3.4535	3.4	1199.96	1060	1199.96	1180	2299.92	2240	2264.31	2.3

Theoretical Calculations:

$$\text{Power} = \sqrt{3} \times V_L \times I_L \times \cos \phi$$

$$\cos \phi = 1$$

$$\text{Power} = \text{Wattage rating of lamp load} \times \text{No of lamps (One lamp is of 100W rating)}$$

$$W_1 = V_L \times I_L \times \cos (30 + \phi)$$

$$\phi = 0$$

$$W_2 = V_L \times I_L \times \cos (30 - \phi)$$

$$\text{Total Power} = P = W_1 + W_2$$



SOMAIYA
VIDYAVIHAR UNIVERSITY

K. J. Somaiya College of Engineering

K. J. Somaiya College of Engineering, Mumbai-77
(A Constituent College of Somaiya Vidyavihar University)
Department of Sciences and Humanities



Conclusion:

The two wattmeter Method proves to be a robust and accurate technique for measuring 3 phase power, ensuring reliable assessment of power consumption in diverse electric systems.

Signature of faculty in-charge with Date: